

Example 6-2


4-to-1 Multiplexer, Using Logic Equations

```
// Module 4-to-1 multiplexer using data flow. logic equation
// Compare to gate-level model
module mux4 to 1 (out, i0, i1, i2, i3, s1, s0);

// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3; // data inputs
input s1, s0;         // selection

//Logic equation for out
assign out = (~s1 & ~s0 & i0) |
             (~s1 & s0 & i1) |
             (s1 & ~s0 & i2) |
             (s1 & s0 & i3) ;

endmodule
```

 

$s_1 s_0$	out
00	i_0
01	i_1
10	i_2
11	i_3

Example 6-3 4-to-1 Multiplexer, Using Conditional Operators

```
// Module 4-to-1 multiplexer using data flow. Conditional operator.
// Compare to gate-level model
module multiplexer4_to_1 (out, i0, i1, i2, i3, s1, s0);

// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;

// Use nested conditional operator
assign out = s1 ? ( s0 ? i3 : i2) : (s0 ? i1 : i0) ;

endmodule
```

Example 6-4 4-bit Full Adder, Using Dataflow Operators

```
// Define a 4-bit full adder by using dataflow statements.
module fulladd4(sum, c_out, a, b, c_in);

// I/O port declarations
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;

// Specify the function of a full adder
assign {c_out, sum} = a + b + c_in;

endmodule
```

 


Figure 6-2 4-bit Ripple Carry Counter

Example 6-6 Verilog Code for Ripple Counter

```
// Ripple counter
module counter(Q , clock, clear);

// I/O ports
output [3:0] Q;
input clock, clear;

// Instantiate the T flipflops
T_FF tff0(Q[0], clock, clear);
T_FF tff1(Q[1], Q[0], clear);
T_FF tff2(Q[2], Q[1], clear);
T_FF tff3(Q[3], Q[2], clear);

endmodule
```

 


Figure 6-4 Negative Edge-Triggered D-flipflop with Clear

Example 6-8 Verilog Code for Edge-Triggered D-flipflop

```
// Edge-triggered D flipflop
module edge_dff(q, qbar, d, clk, clear);

// Inputs and outputs
output q, qbar;
input d, clk, clear;

// Internal variables
wire s, sbar, r, rbar, cbar;

// dataflow statements
// Create a complement of signal clear
assign cbar = ~clear;

// Input latches; A latch is level sensitive. An edge-sensitive
// flip-flop is implemented by using 3 SR latches.
assign sbar = ~(rbar & s),
        s = ~(sbar & cbar & ~clk),
        r = ~(rbar & ~clk & s),
        rbar = ~(r & cbar & d);

// Output latch
assign q = ~(s & qbar),
        qbar = ~(q & r & cbar);

endmodule
```

 


Figure 6-3 T-flipflop

Example 6-7 Verilog Code for T-flipflop

```
// Edge-triggered T-flipflop. Toggles every clock
// cycle.
module T_FF(q, clk, clear);

// I/O ports
output q;
input clk, clear;

// Instantiate the edge-triggered DFF
// Complement of output q is fed back.
// Notice qbar not needed. Unconnected port.
edge_dff ff1(q, ,~q, clk, clear);

endmodule
```

Behavioral level of abstraction

Highest level

Defn (testbench)

a program designed to exercise a digital system to verify its functionality

Notes: 1) written in Verilog at the behavioral level

2) does not verify timing

3) testbenches have 2 purposes

- generate test patterns to exercise the digital design

- collect and output the circuit's response

- (optional) compare outputs with expected outputs

Not everything in Behavioral modeling
is synthesizable



But some of that can be used in testbenches

★
YOU DON'T

SYNTHESIZE

TESTBENCHES

(ONLY DESIGNS)

  

Behavioral models have 2 structured procedures

- initial statements
- always statements

Some observations

- 1) no limit on the number of these in a module
- 2) all of them execute concurrently and begin at time $t=0$.
- 3) cannot nest them

keyword

syntax: initial

[delay] procedural statement

- assignment (blocking or non-blocking)
- continuous assignment
- conditional statement
- case statement
- loop
- event trigger
- parallel block
- wait statement
- disable statement

when there are than 1 procedural statements,

Syntax: initial

begin

=====
=====

Keywords

end

[delay] procedural statement

example of
a sequential
block

initial statements are

not

synthesizable

Example 7-1 initial Statement

```
module stimulus;

reg x,y, a,b, m;

initial
    m = 1'b0; //single statement; does not need to be grouped

initial
begin
    #5 a = 1'b1; //multiple statements; need to be grouped
    #25 b = 1'b0;
end

initial
begin
    #10 x = 1'b0;
    #25 y = 1'b1;
end

initial
    #50 $finish;

endmodule
```

time	statement executed
0	m = 1'b0;
5	a = 1'b1;
10	x = 1'b0;
30	b = 1'b0;
35	y = 1'b1;
50	\$finish;

always statement

- begins executing at time $t=0$
- no limit on the number in a module
- no nesting
- if a sequential block, need begin/end
- operates in a continuous loop
(always means always)

[in contrast, initial states execute
only once...]

what follows is


Very

Important

reg variables can only be assigned values

- when declared
- inside an initial or an always Statement
 
```
module  
  reg a;  
  a = 1'b1;  
endmodule
```



```
module  
  reg a = 1'b1;  
  reg b;  
  
  initial  
    b = 1'b0;  
  
endmodule
```



example 7.5

[Handwritten signature]

always Statement

```
module clock_gen (output reg clock);  
//Initialize clock at time zero  
initial  
    clock = 1'b0;  
//Toggle clock every half-cycle (time period = 20)  
always  
    #10 clock = ~clock;  
initial  
    #1000 $finish;  
endmodule
```

When do they
execute?

```
module FA_Mix (A, B, Cin, Sum, Cout);  
    input A, B, Cin;  
    output Sum, Cout;  
    reg Cout;  
    reg T1, T2, T3;  
    wire S1;  
  
    xor X1 (S1, A, B);           // Gate instantiation.  
  
    always  
        #5 T1 = A & Cin;  
           T2 = B & Cin;  
           T3 = A & B;  
           Cout = (T1 | T2) | T3;  
    end  
  
    assign Sum = S1 ^ Cin;      // Continuous assignment.  
endmodule
```


Two kinds of assignments

- blocking
- non-blocking

- blocking (Syntax: $a = b;$)

LHS updates before next statement executes

- non-blocking (Syntax: $a \leftarrow b;$)

RHS is recorded

LHS updates at the end of
an initial/always procedure

initial
begin
A=3; B=2;
end

initial
begin
#10 A=B;
B=A;
end

A=B=2

initial
begin
A=3; B=2;
end

initial
begin
#10 A<=B;
B<=A;
end

A=2 They swapped
B=3

Rules

- ① do not use non-blocking assignments
in continuous assignment statements
- ② do not mix blocking & non-blocking
in ~~the~~ the same initial/always procedure

you can put #delay on a line by itself

e.g.

always.

begin

#5;

//

A=B;

#10;

C=D;

end

Can use expressions

e.g.

#(on-delay/2) A=B;