 


## Defn (partitioning)

the process of dividing a design into modules thereby creating a

design hierarchy



Can partition

- horizontally

- vertically

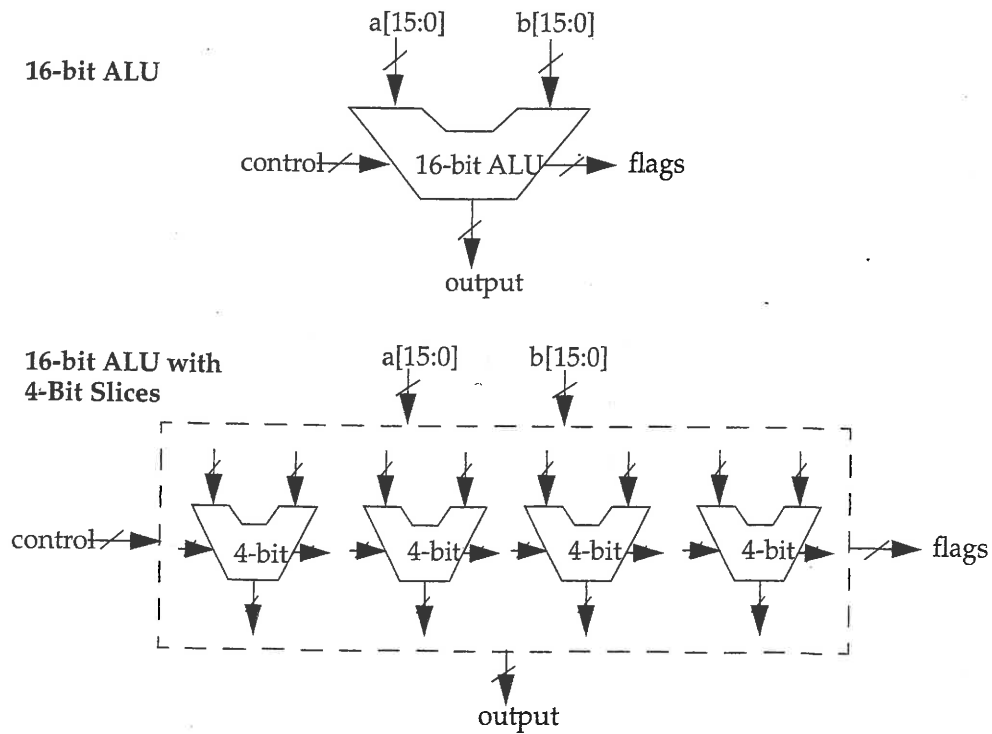


Figure 14-7 Horizontal Partitioning of 16-bit ALU

easier to optimize small bit  
circuitry

 


Figure 14-8 Vertical Partitioning of 4-bit ALU

easier to optimize individual functions

## General partitioning rules

- only leaf nodes in the hierarchy should be gate level of abstraction

makes the synthesis faster

- critical paths should be in one module entirely

defn (critical path)

slowest combination logic path  
between registers

makes timing analysis easier  
and makes it easier to optimize  
the timing

- whenever possible, register the module output


makes it easier to determine timing between modules

- potentially sharable resources should be in the same module


e.g. always @ (A or B or C or Sel)

$$D = \text{sel} ? A + C : A + B;$$

w/o sharing

 

w/sharing

 

- keep modules as small as possible  
(consistent with above guidelines)

2-1

```
module Continuous (StatIn, StatOut);  
  input StatIn;  
  output StatOut;  
  
  assign StatOut = ~ StatIn; // Continuous assignment.  
endmodule  
// Synthesized netlist is shown in Figure
```



2-2


```

module Blocking (Preset, Count);
  input [0:2] Preset;
  output [3:0] Count;
  reg [3:0] Count;

  always @ (Preset)
    Count = Preset + 1;
    // Blocking procedural assignment.
endmodule

```

 // Synthesized netlist is shown in Figure



Count 3 = 0 ✓✓  
 Count 2 = 1 ✓✓  
 Count 1 = 0 ✓✓  
 Count 0 = 0 ✓✓




2-3

```

module NonBlocking (RegA, Mask, RegB);
  input [3:0] RegA, Mask;
  output [3:0] RegB;
  reg [3:0] RegB;

  always @ (RegA or Mask)
    RegB <= RegA & Mask;
    // Non-blocking procedural assignment.
endmodule
// Synthesized netlist is shown in Figure

```

 

2-3

```

module Target (Clk, RegA, RegB, Mask);
  input Clk;
  input [3:0] RegA, Mask;
  output [3:0] RegB;
  reg [3:0] RegB;


```

```

  always @ (posedge Clk)
    RegB <= RegA & Mask;
endmodule

```

 // Synthesized netlist is shown in Figure



2-11


```

module ConstantShift (DataMux, Address);
input [0:3] DataMux;
output [0:5] Address;

    assign Address = (~ DataMux) << 2;
endmodule
// Synthesized netlist is shown in Figure

```

a constant

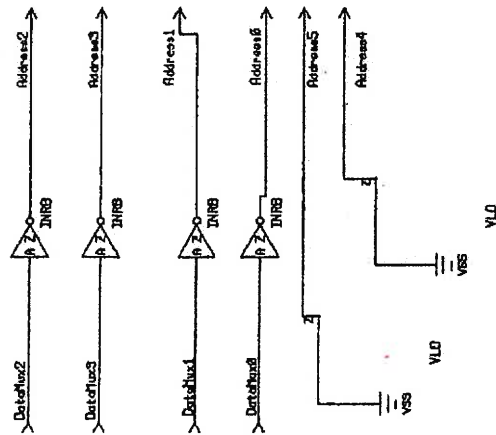

2-12


```

module VariableShift (MemDataReg, Amount, InstrReg);
input [0:2] MemDataReg;
input [0:1] Amount;
output [0:2] InstrReg;

    assign InstrReg = MemDataReg >> Amount;
endmodule
// Synthesized netlist is shown in Figure

```

← a variable

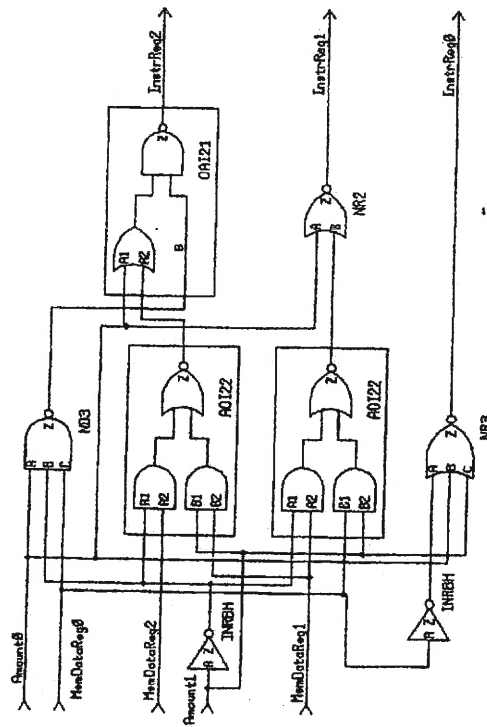


2-12

```

module PartSelect (A, C, ZCat);
  input [3:0] A, C;
  output [3:0] ZCat;

  assign ZCat[2:0] = {A[2], C[3:2]};
endmodule
// Synthesized netlist is shown in Figure .

```

 


```

module NonComputeRight (Data, Index, Dout);
  input [0:3] Data;
  input [1:2] Index;
  output Dout;

  assign Dout = Data [Index];
endmodule
// Synthesized netlist is shown in Figure 2-17.

```

 


**Figure 2-17** Non-constant bit-select generates a multiplexer. (if on RHS)

```

module NonComputeLeft (Mem, Store, Addr);
  output [7:0] Mem;
  input Store;
  input [1:3] Addr;

  assign Mem [Addr] = Store;
endmodule
// Synthesized netlist is shown in Figure

```

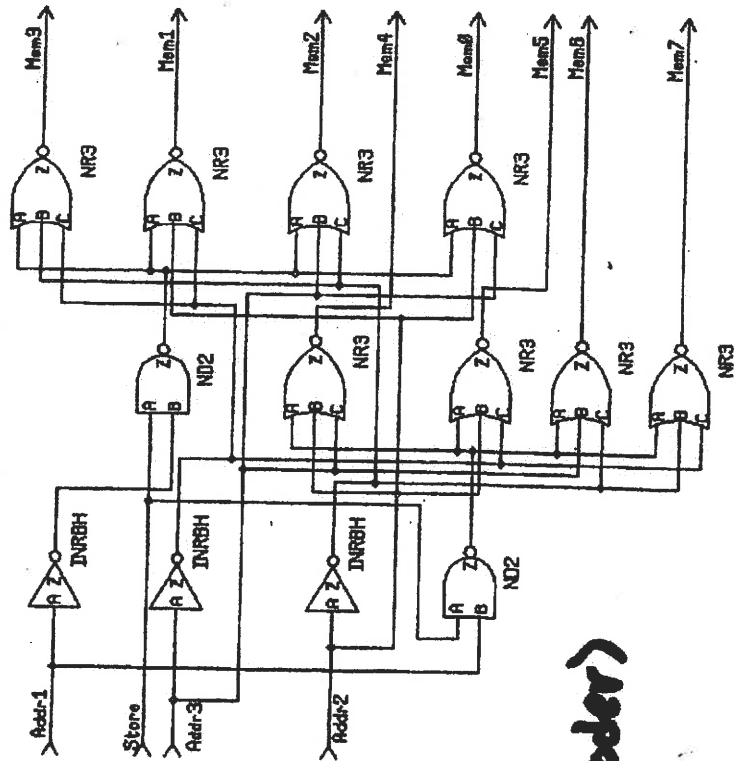

(a decoder)

```

module ConditionalExpression (StartXM, ShiftVal,
                             Reset, StopXM);
    input StartXM, ShiftVal, Reset;
    output StopXM;


```

```

    assign StopXM = (! Reset) ? StartXM ^ ShiftVal :
                    StartXM | ShiftVal;
endmodule

```

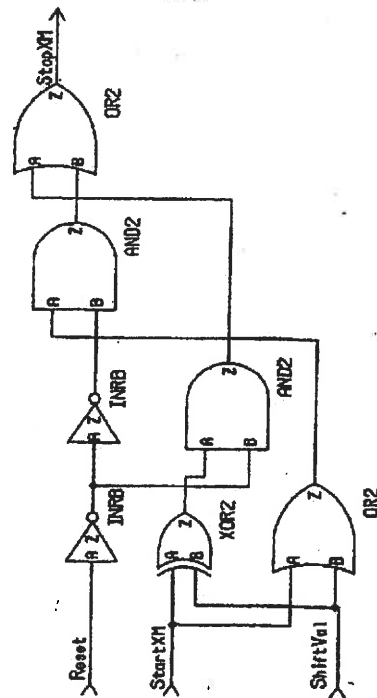// Synthesized netlist is shown in Figure .



⇒ a mux



if-then-else code synthesizes as a  
multiplexer


e.g.:

if (A)

Y = B;

else

Y = C;

 

# Latch inference



a really, really bad thing (really)

Occurs when

- an if-then-else doesn't contain a default else

or

- case statement where not all case values listed  
and

no default

2-26


```

module Compute (Marks, Grade);
    input [1:4] Marks;
    output [0:1] Grade;
    reg [0:1] Grade;

    parameter FAIL = 1, PASS = 2, EXCELLENT = 3;

    always @ (Marks)
        if (Marks < 5)
            Grade = FAIL;
        else if ((Marks >= 5) & (Marks < 10))
            Grade = PASS;
        else
            Grade = EXCELLENT;
    endmodule

```

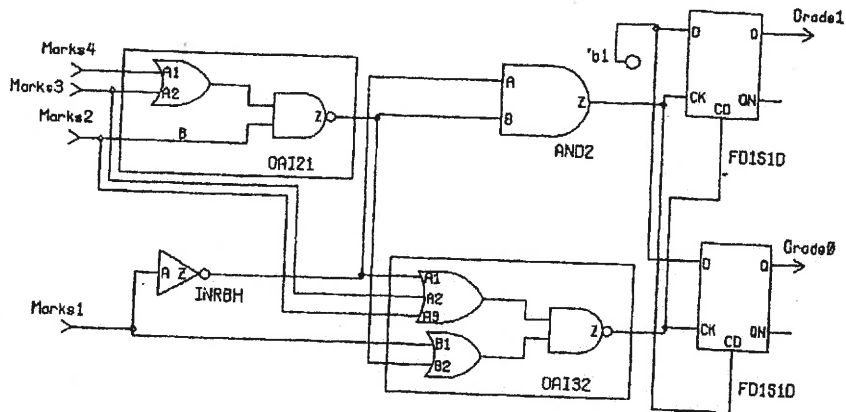

2-26


2-27

```

module ComputeNoLatch (Marks, Grade);
  input [1:4] Marks;
  output [0:1] Grade;
  reg [0:1] Grade;
  parameter FAIL = 1, PASS = 2, EXCELLENT = 3;

  always @ (Marks)
    if (Marks < 5)
      Grade = FAIL;
    else if ((Marks >= 5) && (Marks < 10))
      Grade = PASS;
    else
      Grade = EXCELLENT;
endmodule

```

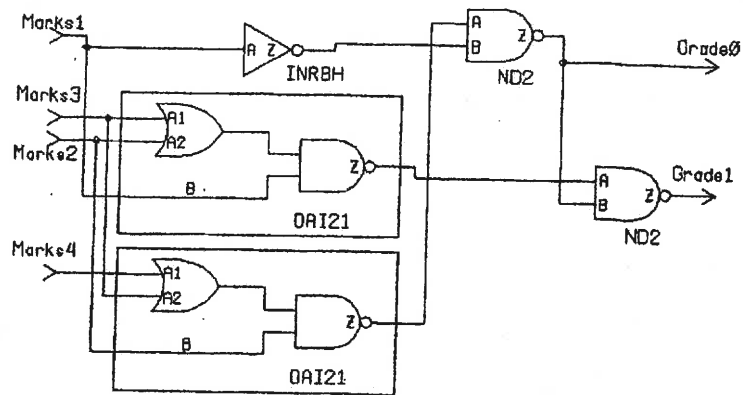


2-27

```

..
always @ (CurrentState)
begin
zip = 0;
case (CurrentState)
..
endcase
end

```

 (a preassignment)  
// This statement added.



```

module StateUpdate (CurrentState, zip);
input [0:1] CurrentState;
output [0:1] zip;
reg [0:1] zip;

parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;

always @ (CurrentState)
case (CurrentState)
S0,
S3: zip = 0;
S1: zip = 3;
endcase
endmodule

```

Consider the following...

parameter s0=0, s1=1, s2=2, s3=3;

always @ (abc)

case (abc) // synthesis full-case

s0, s1: zip=0;

s3: zip=2;

endcase



Known as a

synthesis directive

Prevent latch inference  
w/o

- preassignment
- default in the case statement

when synthesis full-case makes more sense ...

parameter  $S0 = 3'b001$ ,  $S1 = 3'b010$ ,  $S2 = 3'b100$ ;



S0: —

S1: —

S2: —

endcase

```

module PriorityLogic (NextToggle, Toggle);
  input [2:0] Toggle;
  output [2:0] NextToggle;
  reg [2:0] NextToggle;

  always @ (Toggle)
    casez (Toggle)
      3'bxx1 : NextToggle = 3'b010;
      3'bx1x : NextToggle = 3'b110;
      3'blxx : NextToggle = 3'b001;
      default : NextToggle = 3'b000;
    endcase
endmodule


```



```


if (Toggle[0] == 'b1)
  NextToggle = 3'b010;
else if (Toggle[1] == 'b1)
  NextToggle = 3'b110;
else if (Toggle[2] == 'b1)
  NextToggle = 3'b001;
else
  NextToggle = 3'b000;

```

 



2-37

 

```

if (Toggle[0] == 'b1')
    NextToggle = 3'b010;
if (Toggle[1] == 'b1')
    NextToggle = 3'b110;
if (Toggle[2] == 'b1')
    NextToggle = 3'b001;
if ((Toggle[0] == 'b1') &&
    (Toggle[1] == 'b1') &&
    (Toggle[2] == 'b1'))
    NextToggle = 3'b111;

```



```

module ParallelCase (Toggle, NextToggle);
    input [2:0] Toggle;
    output [2:0] NextToggle;
    reg [2:0] NextToggle;


    always @ (Toggle)
        case (Toggle)
            3'bxx1 : NextToggle = 3'b010;
            3'bxx0 : NextToggle = 3'b110;
            3'b1xx : NextToggle = 3'b001;
            default : NextToggle = 3'b000;
        endcase
endmodule

```

2-37
 
### 2.3.2 Priority Decoder using an if/else statement

```
// 2. using an if statement
always @ (sl or a or b or c)
  if (sel == 2'b11)
    d = a;
  else if (sel == 2'b10)
    d = b;
  else
    d = c;
```




## 2.3 Priority Decoders

### 2.3.1 Priority Decoder using a case statement

```
// 1. using a case statement
always @ (sel or a or b or c)
  case (sel)
    2'b11: d = a;
    2'b10: d = b;
    default: d = c;
  endcase
```

1. Both case and if statements result in priority structures.

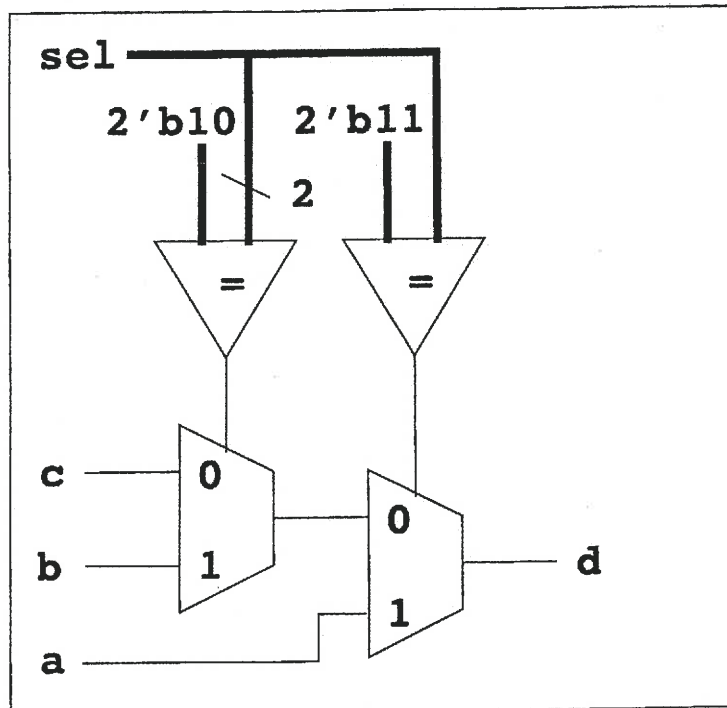2. The order of the variables determines the priority




## 2.4 Parallel Priority Decoders

### 2.4.1 Parallel Priority Decoders Using a Synthesis Directive

```
// using a synthesis directive  
always @ (sl or a or b or c)  
  case (sel) // parallel_case  
    2'b11: d = a;  
    2'b10: d = b;  
    default:d = c;  
  endcase
```

 **Note: full\_case not used**

The **parallel\_case** synthesis directive prevents the cascaded priority logic you get with the if-then-else-if-then....



2-44


```

output [3:0] Line;
reg [3:0] Line;

integer J;

always @ (Address)
  for (J = 3; J >= 0; J = J - 1)
    if (Address == J)
      Line[J] = 1;
    else
      Line[J] = 0;
endmodule

```

 

When the for-loop is expanded, the following four if statements are obtained.

```

if (Address == 3) Line[3] = 1; else Line[3] = 0;
if (Address == 2) Line[2] = 1; else Line[2] = 0;
if (Address == 1) Line[1] = 1; else Line[1] = 0;
if (Address == 0) Line[0] = 1; else Line[0] = 0;

```

~~Rule~~

Law:

Blocking  
assignments



use for  
combinational logic

non-blocking  
assignments



use for  
sequential logic

Consider

reg  $TA, TB;$

always @ (A or B or C)

begin

$TA = A \mid B;$

$TB = TA \& C;$

end

Blocking  
assignments

Synthesizes as



reg TA, TB;

always@ (A or B or C)

begin

TA <= A | B;

TB <= TA & C;

end




uses "old" TA value



need some sort of  
storage...



I want

 

w/Blocking

always@ (posedge clk)


begin

B = A;

C = B;

D = C;

end

 

w/non-blocking

always@ (posedge clk)

begin

B <= A;

C <= B;

D <= C;

end



Assume CLK period = 10 ns  
 Assume  $t_{su} = t_h = 0$

Constraining combinational outputs that drive combinational inputs

